

## Exam in TSEI10/TEN1, Analog Filters

**Time:** 2015-03-19, 14-18

**Place:** U1

**Examiner:** Håkan Johansson

**Aid:** Pocket calculator  
Tables and formulas for analog and digital filters  
Söderkvist: Formler & Tabeller  
Ingelstam, Rönngren, Sjöberg: Tefyma  
Ekbohm: Tabeller & Formler NT  
Nordling: Physics Handbook for Science and Engineering  
Strid: Formler & Lexikon  
Mathematical tables

**Number of problems:** 7

**Instructions:** Maximum 70 points, 30 points required to pass the exam.  
**Note** that a **motivation/solution** is required to get the maximal number of points for a problem!

**Note** that 10, 8, 6, 4, or 2 points obtained at the **seminars** means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.

**Results:** Available 2015-04-02

- 1 a) What does a linear-phase response of an analog filter mean? (2 p)
- b) What are lowpass and highpass notch sections? (2 p)
- c) How is an inductor transformed in a lowpass-to-bandpass frequency transformation? (2 p)
- d) Explain what the gain-bandwidth product of an OP-amplifier is. (2 p)
- e) Why should one generally not use parallel-form structures when implementing analog filters? (2 p)

2) Synthesize a lowpass Chebyshev-I filter that meets the following specification:  $\omega_c = 2\pi \times 20$  krad/s,  $\omega_s = 2\pi \times 52$  krad/s,  $A_{max} = 0.5$  dB, and  $A_{min} = 50$  dB. Determine the poles and zeros, and indicate their locations in the  $s$ -plane. The filter order should not be higher than necessary. (10 p)

3) Realize a highpass Caer filter that meets the following specification:  $\omega_c = 2\pi \times 50$  krad/s,  $\omega_s = 2\pi \times 10$  krad/s,  $A_{max} = 0.1$  dB, and  $A_{min} = 44$  dB. Use a  $\pi$ -type ladder structure. Determine the element values assuming  $R_1 = R_2 = 50\Omega$ . (10 p)

4) Assume that we have a first-order prototype lowpass filter with a transfer function

$$H(S) = \frac{G}{S - S_{LP}}$$

and that we frequency transform this filter into bandpass and bandstop filters.

- a) Determine the zeros and poles of the transformed filters when  $S_{LP} = -2$  and  $\omega_f^2 = 4\pi^2$ . (6 p)
- b) For the bandstop filter, determine the value of  $G$  so that the frequency response equals one for  $\omega = 0$ . (4 p)

5) The transfer function of a second-order filter section can generally be expressed as


$$H(s) = \frac{As^2 + Bs + C}{s^2 + Ds + E}$$

- a) Determine  $A$ ,  $B$ , and  $C$  so that the filter corresponds to a lowpass, highpass, and bandpass filter, respectively. (5 p)
- b) With  $A = 2$ , determine  $B$  and  $C$  so that the filter corresponds to a notch filter with a notch frequency at  $\omega = 2\pi \times 10$  rad/s. (3 p)
- c) State the relation between  $D$  and  $E$  that ensures that the poles form a complex-conjugated pole pair. (2 p)

6) Derive an expression for the transfer function  $H(s) = V_{out}(s)/V_{in}(s)$  for the filter below. What type of filter is it?

a) Assume an ideal OP-amplifier ( $A = \infty$ ). (5 p)

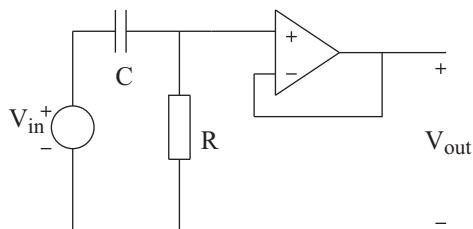b) Assume an OP-amplifier with the transfer function  $A(s) = \frac{A_0}{1 + \frac{s}{\omega_{3dB}}}$ . (5 p)



7) Determine  $Z_{in}(s) = V_1(s)/I_1(s)$  in the terminated two-port below. Also determine the magnitude  $|Z_{in}(j\omega)|$ . What is the function of the terminated two-port? The elements in the chain matrix of the two-port are  $A = C = 2$ ,  $B = -1$ , and  $D = 1$ . The terminating impedance is  $Z_2(s) = 1/s$ . (10 p)

