

Exam in TSEI10/TEN1, Analog Filters

Time: 2015-06-10, 14-18

Place: TER2

Examiner: Håkan Johansson

Aid: Pocket calculator
Tables and formulas for analog and digital filters
Söderkvist: Formler & Tabeller
Ingelstam, Rönngren, Sjöberg: Tefyma
Ekbohm: Tabeller & Formler NT
Nordling: Physics Handbook for Science and Engineering
Strid: Formler & Lexikon
Mathematical tables

Number of problems: 7

Instructions: Maximum 70 points, 30 points required to pass the exam.
Note that a **motivation/solution** is required to get the maximal number of points for a problem!

Note that 10, 8, 6, 4, or 2 points obtained at the **seminars** means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.

Results: Available 2015-06-24

- 1
- What is the difference between passive and active components and filters? (2 p)
 - What is the potential disadvantage of using frequency transformations when synthesizing bandpass and bandstop filters? (2 p)
 - Why do doubly resistively terminated LC-filters have lower sensitivity than singly terminated LC filters? (2 p)
 - What is characteristic of the frequency response of a distributed-element filter, as opposed to lumped-element filters? (2 p)
 - What is an inverting amplifier? How can it be realized using an OP amplifier and resistors? (2 p)
- 2) Synthesize a highpass Chebyshev-I filter that meets the following specification: $\omega_c = 2\pi \times 60$ krad/s, $\omega_s = 2\pi \times 20$ krad/s, $A_{max} = 0.5$ dB, and $A_{min} = 60$ dB. Determine the poles and zeros, and indicate their locations in the s-plane. The filter order should not be higher than necessary. (10 p)
- 3) Realize a lowpass Cauer filter that meets the following specification: $\omega_c = 2\pi \times 30$ krad/s, $\omega_s = 2\pi \times 150$ krad/s, $A_{max} = 0.1$ dB, and $A_{min} = 45$ dB. Use a T-type ladder structure. Determine the element values assuming $R_1 = R_2 = 50\Omega$. (10 p)
- 4) Assume that we have a first-order prototype lowpass filter with a transfer function

$$H(S) = \frac{G}{S - S_{LP}}$$

and that we frequency transform this filter into bandpass and bandstop filters.


- Determine the zeros and poles of the transformed filters, expressed in terms of S_{LP} and the parameter ω_f^2 which is used in the transformations. (6 p)
- Assume that we realize the prototype lowpass filter with a first-order T-type ladder structure, and that we transform this realization into the bandstop filter realization. Show that the inductor, with value L, in the lowpass filter is transformed into a parallel connection of an inductor, with value L, and a capacitor, with value $1/(\omega_f^2 L)$. (4 p)

5) The transfer function of a second-order section can generally be expressed as

$$H(s) = \frac{as^2 + bs + c}{s^2 + ds + e}$$

- Determine a, b, and c so that the filter corresponds to a lowpass, highpass, and bandpass filter, respectively. (5 p)
- What is the relation between d and e that ensures that the poles form a complex-conjugated pole pair? (2 p)
- Express the Q factor in terms of d and e. The Q factor is defined as $Q = -r_p / (2\sigma_p)$ where r_p denotes the pole radius and σ_p denotes the real part of the poles. It is assumed that the poles form a complex-conjugated pole pair. (3 p)

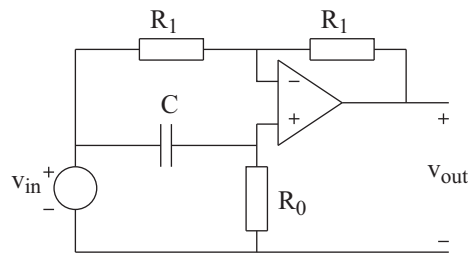6) Determine the transfer function $H(s) = V_{out}(s)/V_{in}(s)$ for the filter below. Assume an ideal OP amplifier. Also determine the poles and zeros, expressed in terms of R_0 and C . What type of filter is it? (10 p)



7) Determine the input impedance $Z_{in}(s) = V_1(s)/I_1(s)$ in the terminated two-port below. The elements in the chain matrix is $A = D = 0$, $B = 1000$, $C = 1$. The terminating impedance is $Z_2(s) = 1/(s \times 10^{-7})$. What is the function of the terminated two-port? (10 p)

