

Exam in TSEI10 Analog Filters

Exam code:	TEN1	
Date:	2016-03-21	Time: 14–18
Place:	TER4	
Examiner:	Håkan Johansson	
Department:	ISY	
Allowed aids:	Pocket calculator Wanhammar: Tables and formulas for analog and digital filters Söderkvist: Formler och Tabeller Ingelstam, Rönngren, Sjöberg: Tefyma Ekbohm: Tabeller och Formler NT Nordling: Physics Handbook for Science and Engineering Strid: Formler och Lexikon Mathematical tables	
Number of tasks:	7	
Grading:	Maximum 70 points, 30 points required to pass the exam. Note that a motivation/solution is required to get the maximal number of points for a problem. Note that 10, 8, 6, 4, or 2 points obtained at the seminars means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.	
Solutions:	Will be published no later than three days after the exam at http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/	
Result:	Available 2016-04-04	

- 1
 - a. Explain the meaning of a linear and time-invariant system (filter). (2 p)
 - b. What is the difference between second-order lowpass, highpass, and bandpass sections, regarding their zero locations? (2 p)
 - c. What are the potential drawbacks of using frequency transformations when designing bandpass and bandstop filters? (2 p)
 - d. Why is it important to use low-sensitivity filter realizations? (2 p)
 - e. Explain what the gain-bandwidth product of an OP amplifier is, and why it is desired to have a large gain-bandwidth product. (2 p)

- 2 Synthesize a Causer filter that meets the following specification: $\omega_c = 2\pi$ Mrad/s, $\omega_s = 2\pi \times 2$ Mrad/s, $A_{\max} = 0.1$ dB ($\rho = 15\%$), and $A_{\min} = 50$ dB. Determine the poles and zeros, and indicate their locations in the s -plane. The filter order should not be higher than necessary. (10 p)

- 3 Realize a highpass Chebyshev-I filter that meets the following specification: $\omega_c = 2\pi \times 5$ Mrad/s, $\omega_s = 2\pi$ Mrad/s, $A_{\max} = 0.5$ dB, and $A_{\min} = 40$ dB. Use a π -type ladder structure. Determine the capacitor and inductor values assuming source and load resistors with the same value according to $R_S = R_L = 2$ k Ω . (10 p)

- 4 The transfer function of a second-order section can generally be expressed as

$$H(s) = \frac{as^2 + bs + c}{s^2 + ds + e}$$


- a. Determine a , b and c (zero or nonzero constants) so that $H(s)$ corresponds to a bandpass filter and a bandstop (notch) filter, respectively. (4 p)
- b. Assume that $a = b = 0$ and $c = e$ which makes $H(s)$ correspond to a lowpass filter with a DC gain of $|H(j0)| = 1$. When $e > d^2/2$, $|H(j\omega)|$ has a maximum value for $\omega = \omega_{peak}$, $0 < \omega_{peak} < \infty$. Determine ω_{peak} and $|H(j\omega_{peak})|$ when $e = 10$ and $d = 1$. (6 p)

- 5 Assume that $H(S)$ is a first-order prototype lowpass filter according to

$$H(S) = \frac{G}{S - P}$$

where G is a gain constant and P is the pole, and assume that $H(S)$ is frequency transformed into bandpass and bandstop filters.

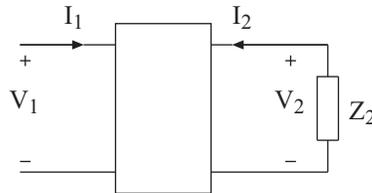- a. Determine the zeros and poles of the bandpass and bandstop filters when $P = -4$ and $\omega_I^2 = 4\pi^2$. (6 p)
- b. Assume that we realize the prototype lowpass filter with a first-order π -type ladder structure, and that we transform this realization into the bandstop filter realization. Show that the capacitor, with the value C , in the lowpass filter is transformed into a series connection of a capacitor, with the value C , and an inductor, with the value $1/(\omega_I^2 C)$. (4 p)
- 6 a. For the terminated two-port below, determine the input impedance $Z_1(s)$ expressed in terms of $Z_2(s)$ and the two-port's chain matrix parameters $A(s)$, $B(s)$, $C(s)$, and $D(s)$. The input impedance is defined by $Z_1(s) = V_1(s)/I_1(s)$. (5 p)
- b. Assume that $Z_2(s) = 10^8/s$ and that A , B , C , and D are real-valued constants. Select values of A , B , C , and D so that the input impedance corresponds to the inductor $Z_1(s) = 10^{-4}s$. (The solution is not unique, suggest one.) (5 p)



- 7 a. Derive the transfer function $H(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$ for the active filter below, and show that it can be written as $H(s) = H_1(s)H_2(s)$ where

$$H_1(s) = \frac{1}{1 + sRC}, \quad H_2(s) = \frac{A(s)}{1 + A(s)}$$

with $A(s)$ being the transfer characteristics of the OP amplifier (that is, a non-ideal OP amplifier is assumed). (5 p)

- b. Determine the 3dB angular frequency for $H_1(s)$, $H_2(s)$, and $H(s)$. Use reasonable approximations if necessary. For a lowpass filter $H(s)$, the 3dB angular frequency, say ω_{3dB} , is defined by $|H(j\omega_{3dB})| = G/\sqrt{2}$ when $|H(j0)| = G$. Assume that $R = 10 \text{ k}\Omega$, $C = 100 \text{ nF}$, and

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

with $A_0 = 10^5$ and $\omega_0 = 2\pi \times 10 \text{ rad/s}$. (5 p)

