

## Exam in TSEI10 Analog Filters

<b>Exam code:</b>	TEN1	
<b>Date:</b>	2016-06-09	<b>Time:</b> 14–18
<b>Place:</b>	TER4	
<b>Examiner:</b>	Håkan Johansson	
<b>Department:</b>	ISY	
<b>Allowed aids:</b>	Pocket calculator Wanhammar: Tables and formulas for analog and digital filters Söderkvist: Formler och Tabeller Ingelstam, Rönngren, Sjöberg: Tefyma Ekbohm: Tabeller och Formler NT Nordling: Physics Handbook for Science and Engineering Strid: Formler och Lexikon Mathematical tables	
<b>Number of tasks:</b>	7	
<b>Grading:</b>	Maximum 70 points, 30 points required to pass the exam. <b>Note</b> that a <b>motivation/solution</b> is required to get the maximal number of points for a problem. <b>Note</b> that 10, 8, 6, 4, or 2 points obtained at the <b>seminars</b> means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.	
<b>Solutions:</b>	Will be published no later than three working days after the exam at <a href="http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/">http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/</a>	
<b>Result:</b>	Available by 2016-06-23	

- 1
- a. What is a main difference between passive and active components? (2 p)
  - b. What is a Richards structure? (2 p)
  - c. What are the potential drawbacks of using frequency transformations when designing bandpass and bandstop filters? (2 p)
  - d. Which of the following two filters requires most components (capacitors and inductors) in a ladder realization: an 11th-order Butterworth or a 7th-order Cauer? (2 p)
  - e. How are the poles and zeros related in an allpass filter? (2 p)
- 2 Synthesize a Cauer filter that meets the following specification:  $\omega_c = 2\pi \times 2$  Mrad/s,  $\omega_s = 2\pi \times 9.4$  Mrad/s,  $A_{\max} = 0.01$  dB ( $\rho = 5\%$ ), and  $A_{\min} = 40$  dB. Determine the poles and zeros, and indicate their locations in the  $s$ -plane. The filter order should not be higher than necessary. (10 p)
- 3 Realize a Butterworth filter that meets the following specification:  $\omega_c = 2\pi \times 10$  Mrad/s,  $\omega_s = 2\pi$  Mrad/s,  $A_{\max} = 0.2$  dB, and  $A_{\min} = 40$  dB. Use a  $T$ -type ladder structure. Determine the capacitor and inductor values assuming source and load resistors with the same value according to  $R_S = R_L = 10$  k $\Omega$ . (10 p)
- 4 Two transfer functions are given as

$$H_1(s) = \frac{p_1}{s + p_1}, \quad H_2(s) = \frac{s}{s + p_2}$$

- a. Determine the poles and zeros (expressed in terms of  $p_1$  and  $p_2$ ) of  $H_3(s)$ , as given below. (4 p)

$$H_3(s) = H_1(s) + H_2(s)$$

- b. Determine the poles and zeros (expressed in terms of  $p_1$  and  $p_2$ ) of  $H_4(s)$ , as given below. (4 p)

$$H_4(s) = H_1(s)H_2(s)$$

- c. Compute the magnitude responses of  $H_3(s)$  and  $H_4(s)$  for the angular frequencies  $\omega = 0$  and  $\omega = \infty$ . (2 p)


- 5 Assume that  $H(S)$  is a first-order prototype lowpass filter according to

$$H(S) = \frac{G}{S - P}$$

where  $G$  is a gain constant and  $P$  is the pole, and assume that  $H(S)$  is frequency transformed into bandpass and bandstop filters.

- a. Determine the zeros and poles of the bandpass and bandstop filters when  $P = -10$  and  $\omega_I^2 = 9$ . (6 p)
- b. Assume that we realize the prototype lowpass filter with a first-order T-type ladder structure, and that we transform this realization into the bandpass filter realization. Show that the capacitor in the lowpass filter, with the capacitance  $C$ , is transformed into a parallel connection consisting of a capacitor, with the capacitance  $C$ , and an inductor, with the inductance  $1/(\omega_I^2 C)$ . (4 p)
- 6 The figure below shows a terminated two-port. Assume that the two-port's chain matrix parameters  $A$ ,  $B$ ,  $C$ , and  $D$  are real-valued constants. Determine values of  $A$ ,  $B$ ,  $C$ , and  $D$ , as well as  $Z_2(s)$ , so that the input impedance corresponds to the inductor impedance  $Z_1(s) = 10^{-4}s$ . The terminating impedance  $Z_2(s)$  should correspond to a capacitor, not an inductor. The input impedance is defined by  $Z_1(s) = V_1(s)/I_1(s)$ . (The solution to this problem is not unique, suggest one possible solution.)

(10 p)

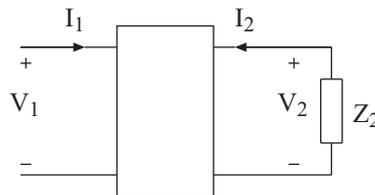

- 7 a. Derive the transfer function  $H(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$  for the active filter below, and show that it can be written as  $H(s) = H_1(s)H_2(s)$  where

$$H_1(s) = \frac{sRC}{1 + sRC}, \quad H_2(s) = \frac{A(s)}{1 + A(s)}$$

with  $A(s)$  being the transfer characteristics of the OP amplifier (that is, a non-ideal OP amplifier is assumed). (5 p)

- b. Sketch the magnitude responses of  $H_1(s)$ ,  $H_2(s)$ , and  $H(s)$ , and indicate their 3dB angular frequencies. Use reasonable approximations if necessary. (For a filter  $H(s)$ , the 3dB angular frequency, say  $\omega_{3dB}$ , is defined by  $|H(j\omega_{3dB})| = G/\sqrt{2}$  where  $G$  represents the maximum value of  $|H(j\omega)|$ ). Assume that  $R = 1 \text{ k}\Omega$ ,  $C = 100 \text{ nF}$ , and

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

with  $A_0 = 10^5$  and  $\omega_0 = 2\pi \times 10 \text{ rad/s}$ . (5 p)

