

## Exam in TSEI10 Filters

<b>Exam code:</b>	TEN1	
<b>Date:</b>	2017-03-13	<b>Time:</b> 14–18
<b>Place:</b>	KÅRA	
<b>Examiner:</b>	Håkan Johansson	
<b>Department:</b>	ISY	
<b>Allowed aids:</b>	Pocket calculator Wanhammar: Tables and formulas for analog and digital filters Söderkvist: Formler och Tabeller Ingelstam, Rönngren, Sjöberg: Tefyma Ekbohm: Tabeller och Formler NT Nordling: Physics Handbook for Science and Engineering Strid: Formler och Lexikon Mathematical tables	
<b>Number of tasks:</b>	7	
<b>Grading:</b>	Maximum 70 points, 30 points required to pass the exam. <b>Note</b> that a <b>motivation/solution</b> is required to get the maximal number of points for a problem. <b>Note</b> that 10, 8, 6, 4, or 2 points obtained at the <b>seminars</b> means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.	
<b>Solutions:</b>	Will be published no later than three days after the exam at <a href="http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/">http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/</a>	
<b>Result:</b>	Available 2017-03-27	

- 1**
- a. Explain why it is important to use low-sensitivity filter structures. (2 p)
  - b. Explain what the gain-bandwidth product of an OP amplifier is, and why it is desired to have a large gain-bandwidth product. (2 p)
  - c. Which of the following two filters requires most inductors in a  $\pi$ -type lowpass ladder structure: a 7th-order Chebyshev-I or a 5th-order Cauer? (2 p)
  - d. What is the relation between the poles and zeros in an allpass filter? (2 p)
  - e. Sketch typical magnitude responses, and pole/zero configurations, of second-order lowpass and highpass notch sections. (2 p)
- 2** Synthesize a Cauer filter that meets the following specification:  $\omega_c = 1$  Mrad/s,  $\omega_s = 2$  Mrad/s,  $A_{\max} = 0.1$  dB ( $\rho = 15\%$ ), and  $A_{\min} = 50$  dB. Determine the poles and zeros, and indicate their locations in the  $s$ -plane. The filter order should not be higher than necessary. (10 p)
- 3** Realize a Chebyshev-I filter that meets the following specification:  $\omega_{c1} = 2\pi \times 10$  krad/s,  $\omega_{c2} = 2\pi \times 12$  krad/s,  $\omega_{s1} = 2\pi \times 8$  krad/s,  $\omega_{s2} = 2\pi \times 15$  krad/s,  $A_{\max} = 0.5$  dB, and  $A_{\min} = 30$  dB. Use a T-type ladder structure. Determine the capacitor and inductor values assuming source and load resistors with the same value according to  $R_S = R_L = 100 \Omega$ . (10 p)
- 4** Assume two (normalized) filters with transfer functions as:

$$H_1(s) = \frac{s}{s^2 + 20s + 116}, \quad H_2(s) = \frac{-s}{s^2 + 8s + 116}$$

- a. Compute the poles and zeros of the overall filter  $H(s)$  when  $H_1(s)$  and  $H_2(s)$  are cascade connected, i.e.,  $H(s) = H_1(s)H_2(s)$ . (4 p)
- b. Compute the poles and zeros of the overall filter  $H(s)$  when  $H_1(s)$  and  $H_2(s)$  are parallel connected, i.e.,  $H(s) = H_1(s) + H_2(s)$ . (4 p)
- c. For each of the two cases above, determine  $H(j\omega)$  for  $\omega = 0$  and  $\omega = \infty$  and state the type of filter (lowpass, highpass, bandpass, or bandstop). (2 p)

- 5 The transfer function of a second-order filter section is given as

$$H(s) = \frac{r_p^2}{s^2 + \frac{r_p}{Q}s + r_p^2}$$


- a. Is this a lowpass, highpass, bandpass, or bandstop filter section? Motivate the answer by sketching the principle behavior of the frequency response. (2 p)
- b. Express in terms of  $r_p$  and  $Q$ , the angular frequency  $\omega > 0$  (say  $\omega_{\text{peak}}$ ) for which the magnitude response  $|H(j\omega)|$  has its maximum. It is assumed here that  $Q > 1/\sqrt{2}$ . (6 p)
- c. Show that  $|H(j\omega_{\text{peak}})| \approx Q$  when  $Q \gg 1$ . (2 p)
- 6 a. Derive the transfer function  $H(s) \triangleq V_{\text{out}}(s)/V_{\text{in}}(s)$  for the active circuit below, expressed in terms of  $Z_1(s)$ ,  $Z_2(s)$  and  $A(s)$ , where  $A(s)$  is the transfer characteristics of the OP amplifier. The OP amplifier is thus non-ideal, but its input impedance can be assumed to be infinite in the derivations. (5 p)

- b. Assume that  $Z_2(s)/Z_1(s) = G$ , with  $Z_1(s)$  and  $Z_2(s)$  being real-valued constants, and thus  $G$  being a real-valued constant. This means that the circuit is an inverting amplifier. However, due to the non-ideal OP amplifier,  $H(s)$  has a lowpass filter frequency response. Determine the 3dB angular frequency for  $H(s)$ , expressed in terms of  $G$ ,  $A_0$ , and  $\omega_0$  (see the OP-amp model below). Use reasonable approximations if necessary. For a lowpass filter  $H(s)$ , the 3dB angular frequency, say  $\omega_{3dB}$ , is defined by  $|H(j\omega_{3dB})| = |H(j0)|/\sqrt{2}$ . Assume that

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

and  $A_0 \gg G$ .

(5 p)

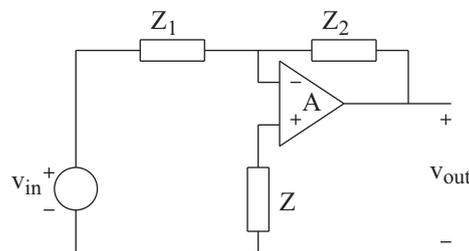

- 7
- a. For the terminated two-port below, determine the input impedance  $Z_1(s) \triangleq V_1(s)/I_1(s)$ , expressed in terms of  $Z_2(s)$  and the two-port's chain matrix entries  $A(s)$ ,  $B(s)$ ,  $C(s)$ , and  $D(s)$ . (5 p)
- b. Assume that it is desired to realize an inductor according to  $Z_1(s) = 10^{-4}s$ . Select  $Z_2(s)$  and real values of  $A$ ,  $B$ ,  $C$ , and  $D$  so that the desired  $Z_1(s)$  is realized. The impedance  $Z_2(s)$  should correspond to a capacitor. The solution is not unique, suggest one. (5 p)

