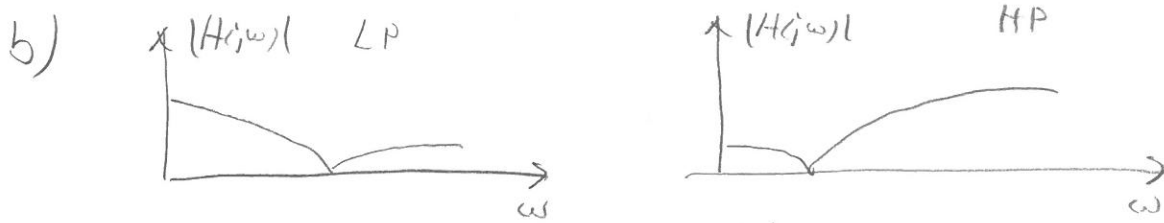


Exam in Analog Filters TSE110 2015-03-19 - SOLUTIONS

a) Linear phase  $\phi(\omega) = -k \cdot \omega$  All freq. components delayed by the same amount



d)  $\omega_T = A_0 \cdot \omega_{3dB}$        $A(s) = \frac{A_0}{1 + \frac{s}{\omega_{3dB}}}$

e) Very sensitive to component variations

2) Order  $N = 5$

Normalized poles

- $0,3623196$
- $0,111963 \pm j 1,0115574$
- $0,2931227 \pm j 0,625177$

Zeros  $s$  at  $s = \infty$

Denormalized poles (mult. by  $\omega_c$ )

- $(- 0,4553043) \times 10^5$
- $(- 0,1406968 \pm j 1,271160) \times 10^5$
- $(- 0,3683489 \pm j 0,7856204) \times 10^5$

Zeros  $s$  at  $s = \infty$

3) Order  $N = 3$ , Use  $A_{max} = 0,09833$  @  $r^2 = 1$  table

$$\left( \omega_c = \frac{\omega_s^2}{\omega_c} \mid \text{set } \omega_s^2 = \omega_c \mid = 1 \quad \omega_s = \frac{\omega_c^2}{\omega_s} = \frac{\omega_c}{\omega_s} = 5 \Rightarrow N = 3 \right)$$


$$N = 3, A_{max} = 0,09833, A_{min} \geq 44, \frac{R_s}{R_c} \leq 5 \Rightarrow 12 \leq \theta \leq 14$$

Choose  $\theta = 13 \Rightarrow$

$$L'_1 = L'_3 = 1,002943$$

$$L'_2 = 0,834496$$

$$L'_2 = 1,107291$$

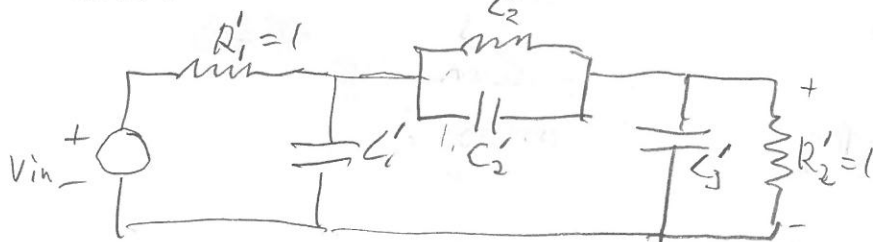


Denormalize ( $R_c = 1$ ):  $L = \frac{L'}{R_i}, C = C' \cdot R_i$

LP  $\rightarrow$  HP  $R_1 = R_2 = 50 \Omega$

$$L_1 = L_3 = \frac{R_1}{\omega_c \cdot C'_1} = 0,158688 \text{ mH}$$

$$L_2 = 4,61372 \text{ mH}$$
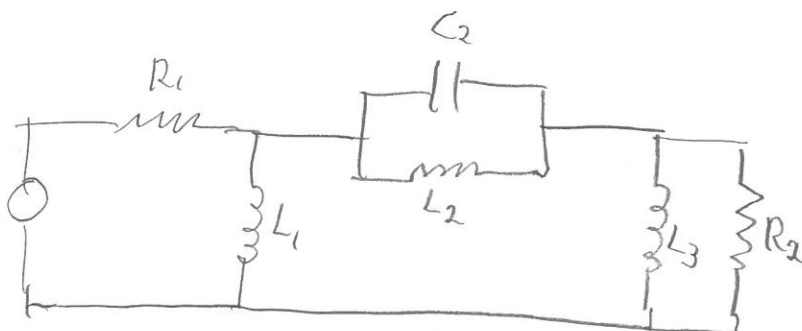
$$C_2 = \frac{1}{R_1 \cdot \omega_c \cdot L'_2} = 57,4934 \text{ nF}$$



$$4a) \text{ BP: } s + \frac{\omega_F^2}{s} - S_{LP} = 0 \Leftrightarrow s^2 - S_{LP} \cdot s + \omega_F^2 = 0$$

$$\Rightarrow \text{poles at } \frac{S_{LP}}{2} \pm \sqrt{\frac{S_{LP}^2}{4} - \omega_F^2} = -1 \pm \sqrt{1 - 4\pi^2}$$

$$= -1 \pm j \sqrt{4\pi^2} \approx -1 \pm j \cdot 6,283185$$

$$\text{zeros at } 0 \text{ and } \infty \quad \left( s + \frac{\omega_F^2}{s} - \infty = 0 \right)$$

$$\text{BS: } \frac{\omega_F^2}{s + \frac{\omega_F^2}{s}} - S_{LP} = 0 \Leftrightarrow \frac{\omega_F^2 \cdot s}{s^2 + \omega_F^2} - S_{LP} = 0$$

$$\Leftrightarrow S_{LP} \cdot s^2 - \omega_F^2 \cdot s + \omega_F^2 \cdot S_{LP} = 0$$

$$\Leftrightarrow s^2 - \frac{\omega_F^2}{S_{LP}} s + \omega_F^2 = 0$$

$$\Rightarrow \text{Poles at } \frac{\omega_F^2}{2 \cdot S_{LP}} \pm \sqrt{\left(\frac{\omega_F^2}{2 \cdot S_{LP}}\right)^2 - \omega_F^2} = -\pi^2 \pm \sqrt{\pi^4 - 4\pi^2}$$

$$\approx -\pi^2 \pm \pi \cdot \sqrt{\pi^2 - 4} \approx -2,25834 \text{ and } -17,4808$$

$$\text{zeros at } \pm j \omega_F = \pm j 2\pi \approx \pm j 6,283185 \quad (s^2 + \omega_F^2 = 0)$$

$$b) H_{BS}(s) = \frac{\zeta}{\frac{\omega_F^2 \cdot s}{s^2 + \omega_F^2} - S_{LP}} \Rightarrow H_{BS}(0) = \frac{\zeta}{-S_{LP}} = 1 \text{ if } \zeta = -S_{LP} = 2$$

$$5a) \text{ LP: } A=B=0, C \neq 0; \text{ HP } B=C=0, A \neq 0$$

$$\text{BP: } A=C=0, B \neq 0$$

$$b) \underbrace{2(\omega_0)^2}_{B=0} + C = 0 \Leftrightarrow -2\omega_0^2 + C = 0 \Rightarrow C = 2 \cdot (2\pi \cdot 10)^2 = 800\pi^2$$

$$c) \text{ poles: } -\frac{D}{2} \pm \sqrt{\left(\frac{D}{2}\right)^2 - E} \text{ complex if } E > \left(\frac{D}{2}\right)^2$$

$$6a) V_+ = V_- = V_{out} = V_{in} \cdot \frac{R}{R + \frac{1}{sC}} \Rightarrow$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{RC \cdot s}{1 + RCs} = \frac{s}{s + \frac{1}{RC}}$$

HP filter

$$= V_{out}(s)$$

$$b) V_{out}(s) = A(s) \cdot [V_+(s) - V_-(s)] = A(s)V_+(s) - A(s)V_{out}(s)$$

$$\Rightarrow V_{out}(s) = \frac{A(s)}{1 + A(s)} \cdot V_+(s) \Rightarrow$$

$$= V_{in}(s) \cdot \frac{s}{s + \frac{1}{RC}}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s}{s + \frac{1}{RC}} \cdot \frac{A(s)}{1 + A(s)} \quad \Rightarrow \text{BP filter}$$

HP          //          LP

$$\frac{A(s)}{1 + A(s)} = \frac{A_0}{1 + \frac{s}{\omega_{3dB}}} = \frac{A_0}{1 + A_0 + \frac{s}{\omega_{3dB}}}$$

$$= \frac{A_0}{1 + A_0} \approx 1 \text{ for } \omega = 0$$

$$\rightarrow 0 \text{ when } \omega \rightarrow \infty$$

$$7/ \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} = \left. \begin{matrix} V_2 = -I_2 Z_2 \\ \phantom{V_2 = -I_2 Z_2} \end{matrix} \right| = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ Z_2 \end{pmatrix}$$

$$\Rightarrow Z_{in}(s) = \frac{V_1(s)}{I_1(s)} = \frac{(A(s) + \frac{B(s)}{Z_2(s)}) V_2(s)}{(C(s) + \frac{D(s)}{Z_2}) V_2(s)} = \frac{2 - s}{2 + s}$$

Allpass filter,  $|Z_{in}(j\omega)| \cong 1$  for all  $\omega$