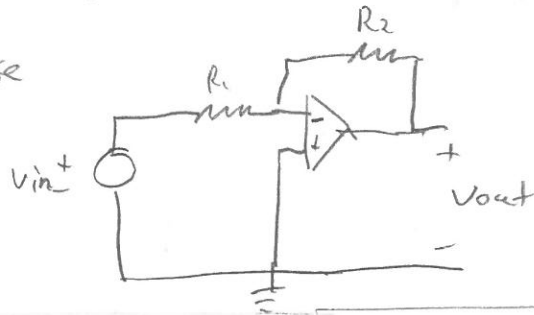


Solutions to TSE110 Analog Filters 150610

- 1a) Passive - can only dissipate power, always stable
 Active - can generate power, can become unstable
- b) May have to be overdesigned due to passb./stopb. symmetry requirements and only one A_{max} & A_{min}
- c) Can be designed using max. power transfer principle
- d) periodic freq. response

e) $V_{out} = -\frac{R_2}{R_1} V_{in}$



2) $\Omega_c = \frac{\omega_F^2}{\omega_c} \left\{ \text{set } \omega_F^2 = \omega_c \right\} = (1, \sqrt{2}, \sqrt{3}, \sqrt{4}, \sqrt{5}) = \frac{\omega_F^2}{\omega_c} = \frac{\omega_c}{\omega_F} = 3 \Rightarrow N=5$

- Normalized poles
- 0,3623196
 - 0,111963 ± j1,0115379
 - 0,2931227 ± j0,625177

zeros 5 at $s = \infty$

Denormalized poles/zeros the same since $\Omega_c = 1$

LP → HP $s = \frac{\omega_F^2}{s} = \frac{\omega_c}{s}$

- poles
- $1,040493 \times 10^6$
 - $(-0,0407505 \pm j0,3681734) \times 10^6$
 - $(-0,2317792 \pm j0,4943423) \times 10^6$

zeros 5 at $s = 0$

$$4a) \text{ BP: } s + \frac{\omega_F^2}{s} - S_{LP} = 0 \Leftrightarrow s^2 - S_{LP} \cdot s + \omega_F^2 = 0 \Rightarrow$$

$$\text{poles at } \frac{S_{LP}}{2} \pm \sqrt{\frac{S_{LP}^2}{4} - \omega_F^2}$$

$$\text{zeros at } s=0 \text{ \& } s=\infty \left(s + \frac{\omega_F^2}{s} - \infty = 0 \right)$$

$$\underline{\text{BS:}} \quad \frac{\omega_F^2}{s + \frac{\omega_F^2}{s}} - S_{LP} = 0 \Leftrightarrow \frac{\omega_F^2 \cdot s}{s^2 + \omega_F^2} - S_{LP} = 0$$

$$\Leftrightarrow S_{LP} \cdot s^2 - \omega_F^2 \cdot s + \omega_F^2 \cdot S_{LP} = 0$$

$$\Leftrightarrow s^2 - \frac{\omega_F^2}{S_{LP}} \cdot s + \omega_F^2 = 0 \Rightarrow$$

$$\text{poles at } \frac{\omega_F^2}{2S_{LP}} \pm \sqrt{\left(\frac{\omega_F^2}{2S_{LP}}\right)^2 - \omega_F^2}$$

$$\text{zeros at } s = \pm j \omega_F \quad (s^2 + \omega_F^2 = 0)$$

$$b) \quad sL \rightarrow \frac{\omega_F^2 \cdot L}{s + \frac{\omega_F^2}{s}} = \frac{1}{\frac{s}{\omega_F^2 L} + \frac{1}{sL}} = \frac{1}{\frac{1}{z_1} + \frac{1}{z_2}}$$

$$\text{with } z_1 = \frac{\omega_F^2 L}{s}, \quad z_2 = sL$$

$$= \frac{1}{sL} \text{ with } L = \frac{1}{\omega_F^2 L}$$

Parallel connection of z_1 & z_2

$$5a) \text{ LP: } a=b=0, c \neq 0 \quad \text{HP: } b=c=0, a \neq 0 \quad \text{BP: } a=c=0, b \neq 0$$

$$b) \text{ Poles at } -\frac{d}{2} \pm \sqrt{\left(\frac{d}{2}\right)^2 - e} \quad \text{complex if } e > \left(\frac{d}{2}\right)^2$$

$$c) -2\sigma_p = d, \quad r_p^2 = e \Rightarrow \alpha = \frac{\sqrt{e}}{d}$$