

1a) Passive - can only dissipate power
 \Rightarrow Passive filters always stable


b) Cascaded two-ports

c) Overdesigned (higher filter order) due to band edge symmetries and the same attenuation in both passbands/stopbands.
 BS BP

d) 11th-order Butterworth - 11 components
 7th-order Chebyshev - 10 components

e) $z = p$ mirrored, $z = a + jb$, $p = -a + jb$

Ex second-order

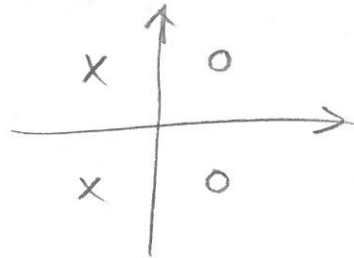

2) Filter order (Nomogram $\frac{\omega_s}{\omega_c} = 4,7$) $N = 4$
 Table C040504) $14 \leq \theta \leq 23$ Select $\theta = 18$ (for ex.)

Normalized poles (rounded) $-0,3749 \pm j1,3374$
 $-0,9954 \pm j0,5928$

zeros $\pm j3,8206$
 2 at ∞


Denormalize, mult. by $\omega_c \Rightarrow$

poles $(-4,711 \pm j16,8062) \times 10^6$
 $(-12,5086 \pm j7,4493) \times 10^6$

zeros $48,0111 \times 10^6$
 2 at ∞

3) LP prototype $\Omega_c = \frac{\omega_F^2}{\omega_c} = 1$ (use $\omega_F^2 = \omega_c$), $\Omega_s = \frac{\omega_s^2}{\omega_c} = 10$

Filter order (Nomogram) $N = 3$

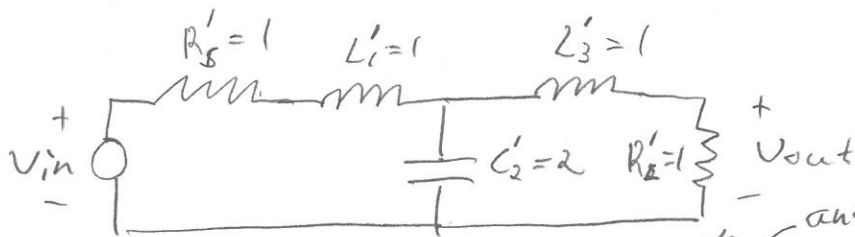


Denormalize with $\Omega_c = 1$, $\epsilon = 0,2$ and $R = R_L = R_S = 10k\Omega$
 $A_{max} = 10 \cdot \log_{10}(1 + \epsilon^2) = 0,2$

$$\epsilon = \sqrt{10^{0,1 A_{max}} - 1} = 0,2171 \Rightarrow \epsilon^{-1/3} = 1,664$$

$$\Rightarrow L_1 = L_3 = 6,010 \text{ kH}, C_2 = 0,1202 \text{ mF}$$

LP \rightarrow HP

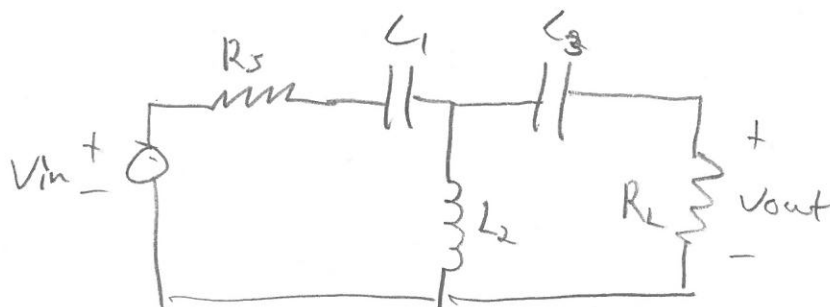

$$C_1 = C_3 = \frac{1}{\omega_F^2 L_1} = 2,648 \text{ pF}$$

$$L_2 = \frac{1}{\omega_F^2 C_2} = 0,1324 \text{ mH}$$

$$4a) H_3(s) = \frac{P_1}{s+P_1} + \frac{s}{s+P_2} = \frac{P_1(s+P_2) + s(s+P_1)}{(s+P_1)(s+P_2)} = \frac{s^2 + 2P_1s + P_1P_2}{(s+P_1)(s+P_2)}$$

poles: $-P_1$ & $-P_2$

zeros: $s = -P_1 \pm \sqrt{P_1^2 - P_1P_2}$

$$b) H_4(s) = \frac{P_1}{s+P_1} \cdot \frac{s}{s+P_2} \quad \text{poles: } -P_1 \text{ & } -P_2$$

zeros: 0 & ∞

c) $|H_3(j0)| = |1+0| = 1$, $|H_3(j\infty)| = |0+1| = 1$

$|H_4(j0)| = |1 \cdot 0| = 0$, $|H_4(j\infty)| = |0 \cdot 1| = 0$

5a) BP: $s + \frac{\omega_I^2}{s} - p = 0 \Leftrightarrow s^2 - p \cdot s + \omega_I^2 = 0$

poles at $\frac{p}{2} \pm \sqrt{\frac{p^2}{4} - \omega_I^2} = \left(p = -10, \omega_I^2 = 9 \right) = -5 \pm 4 = -9, -1$

zeros at $s=0$ & $s=\infty$ ($s^2 + \frac{\omega_I^2}{s} - \infty = 0$)

BS: $\frac{\omega_I^2}{s + \frac{\omega_I^2}{s}} - p = 0 \Leftrightarrow \frac{\omega_I^2 s}{s^2 + \omega_I^2} - p = 0 \Leftrightarrow$

$\Leftrightarrow p s^2 - \omega_I^2 s + \omega_I^2 p = 0 \Leftrightarrow s^2 - \frac{\omega_I^2}{p} s + \omega_I^2 = 0$

\Rightarrow Poles at $\frac{\omega_I^2}{2p} \pm \sqrt{\left(\frac{\omega_I^2}{2p}\right)^2 - \omega_I^2} = 0,45 \pm j 2,966$

zeros at $s = \pm j \omega_I^2 = \pm j 3$

b) BP: $\frac{1}{sL} \rightarrow \frac{1}{(s + \frac{\omega_I^2}{s})L} = \frac{1}{sL + \frac{\omega_I^2 L}{s}} =$

$\Leftrightarrow \frac{\omega_I^2 s}{s^2 + \omega_I^2} = \infty$
 $\Leftrightarrow s^2 + \omega_I^2 = 0$

$= \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$ with $\frac{1}{Z_1} = sL \Leftrightarrow Z_1 = \frac{1}{sL}$

Impedance of parallel connection of Z_1 & Z_2

$\frac{1}{Z_2} = \frac{\omega_I^2 L}{s} \Leftrightarrow Z_2 = \frac{s}{\omega_I^2 L}$

with $L = \frac{1}{\omega_I^2 C}$

$$6) \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} = \begin{pmatrix} -I_2 = \frac{V_2}{Z_2} \\ \frac{V_2}{Z_2} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} 1 \\ 1/Z_2 \end{pmatrix} \cdot V_2$$

$$\Rightarrow Z_{in} = \frac{V_1}{I_1} = \frac{A + \frac{B}{Z_2}}{C + \frac{D}{Z_2}}$$

$$Z_2(s) = \frac{1}{s \cdot C_1}$$


Capacitor

Select $A = D = 0 \Rightarrow$

$$\Rightarrow Z_{in}(s) = \frac{B \cdot C_1 \cdot s}{C} \stackrel{\text{according to problem}}{=} 10^{-4} s$$

Select for ex. $C_1 = 1 \text{ nF}$, $B = 10^5$, $C = 1$

7a)

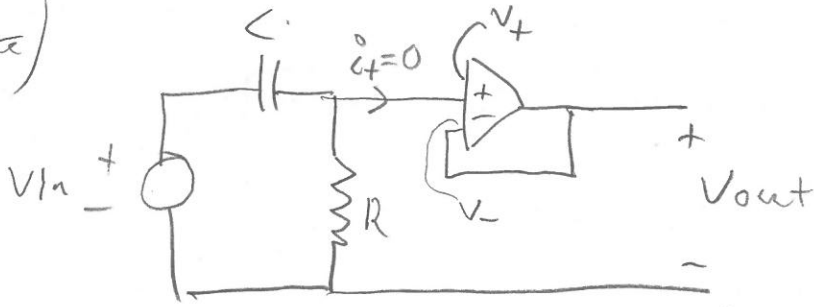

$$V_{out}(s) = A(s) (V_+(s) - V_-(s)) \quad (1)$$

$$V_+(s) = V_{in}(s) \cdot \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} \cdot V_{in}(s) \quad (2)$$

↑
voltage divider

$$V_-(s) = V_{out}(s) \quad (3)$$

$$(1) - (3) \Rightarrow V_{out}(s) = A(s) (H_1(s)V_{in}(s) - V_{out}(s))$$

$$\Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{H_1(s) \cdot A(s)}{1 + A(s)H_2(s)} = H_1(s)H_2(s)$$

$$b) H_1(j\omega) = \frac{j\omega RC}{1 + j\omega RC} \quad \omega_{3dB} = \omega RC = 1 \Rightarrow \omega_{3dB} = \frac{1}{RC} = 10 \text{krad/s}$$

$$\text{max: } |H(j\omega)| = 1$$

$$H_2(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)} = \frac{A_0}{1 + \frac{A_0}{1 + j\omega/\omega_0}} \approx \frac{A_0}{A_0 + 1 + j\omega/\omega_0}$$

$A_0 \gg 1$

$$\omega_{3dB}: \frac{\omega}{\omega_0} = 1 + A_0 \Rightarrow \omega_{3dB} = \omega_0(1 + A_0) \approx \omega_0 A_0 = 277 \text{Mrad/s}$$

