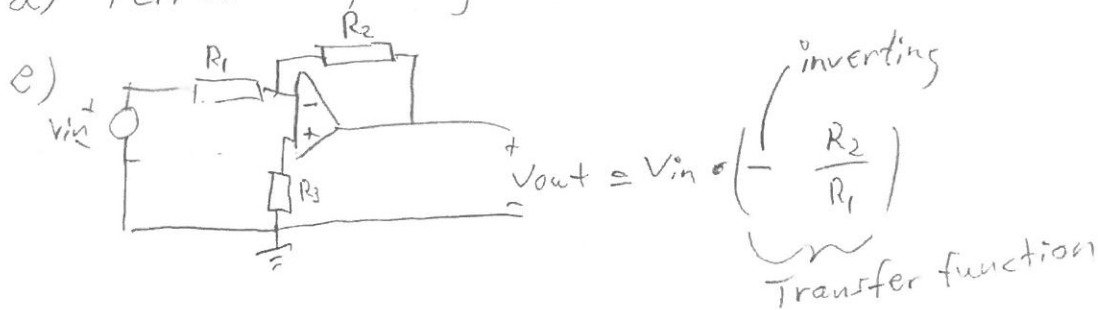


TSE110 Filters - Solutions 170608

- 1/a) Passive - can only dissipate power, always stable filters
 Active - can generate power, can be unstable
- b) Spec. may have to be sharpened \Rightarrow higher filter order
- c) Maximum power transfer principle \Rightarrow lower sensitivity
- d) Periodic frequency response



2) HP filter spec. \Rightarrow ZP:

$$\omega_c = \frac{\omega_F^2}{\omega_c} \quad \left| \text{select } \omega_F^2 = \omega_c \right| = 1, \quad \omega_s = \frac{\omega_F^2}{\omega_s} = \frac{\omega_c}{\omega_s} = 3$$

\Rightarrow Filter order $N=4$

Normalized poles: $-0,175353 \pm j 1,0162529$
 $-0,4233398 \pm j 0,420946$


zeros: 4 at $s = \infty$

Denormalized = Normalized due to $\omega_c = 1$

LP \rightarrow HP $s = \frac{\omega_F^2}{s} = \frac{\omega_c}{s} \Rightarrow$


poles: $(-0,124317 \pm j 0,720473) \times 10^6$
 $(-0,893566 \pm j 0,890502) \times 10^6$

zeros: 4 at $s = 0$

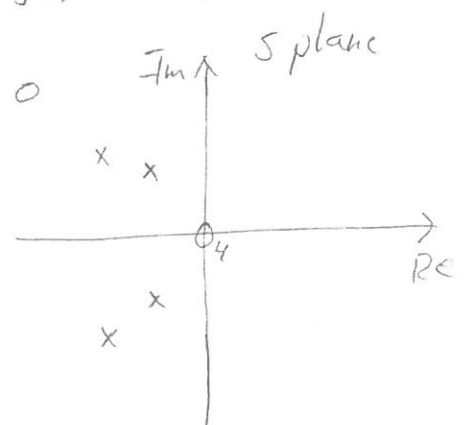

$$3) \frac{\omega_s}{\omega_c} = 5 \Rightarrow N = 3$$

Table C0315 θ , $12 \leq \theta \leq 15$
 Select (for ex.) $\theta = 13 \Rightarrow$

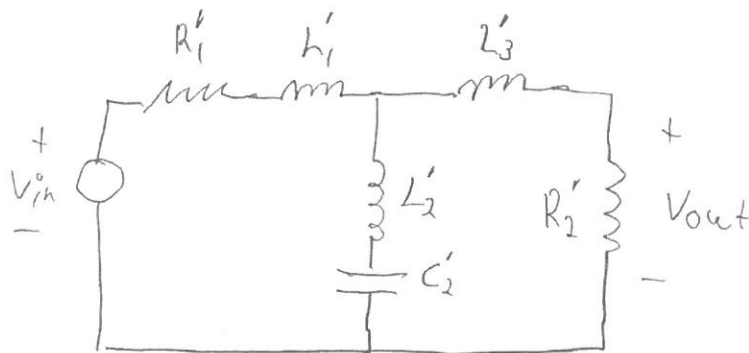

$$R'_1 = R'_2 = 1 \Omega$$

$$L'_1 = L'_3 = 1,002943 \text{ H}$$

$$L'_2 = 0,034496 \text{ H}$$

$$C'_2 = 1,107291 \text{ F}$$

Denormalize $L \rightarrow L \cdot \frac{R_1}{\omega_c}$, $C \rightarrow C \cdot \frac{1}{\omega_c R_1}$, $R_1 = R_2 = 50 \Omega$

$$\Rightarrow L_1 = L_3 = 1,33019 \times 10^{-4} \text{ H}$$

$$L_2 = 4,37517 \times 10^{-6} \text{ H}$$

$$C_2 = 5,87436 \times 10^{-8} \text{ F}$$


4a) $H(s) = H_1(s)H_2(s) = - \frac{s^2}{(s^2 + 24s + 169)(s^2 + 10s + 169)}$
 poles at $-12 \pm j5$ poles at $-5 \pm j12$ 2 zeros at $s=0$

b) $H(s) = H_1(s) + H_2(s) = - \frac{14s^2}{(s^2 + 24s + 169)(s^2 + 10s + 169)}$

\therefore Same poles and zeros as in a).

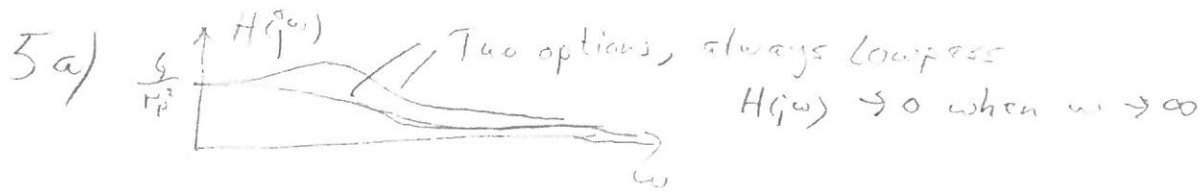c) Same filter in both cases, except for the gain of 14 in b)

$H(j\omega) = 0$, $H(j\infty) = 0$ \therefore Bandpass filter



b) $H(j0) = \frac{G}{r_p^2}$, $G = r_p^2 \Rightarrow H(j0) = 1$ and thus $|H(j\omega)| = 1$

c) $|H(j\omega)| = \frac{|G|}{\sqrt{(r_p^2 - \omega^2)^2 + a^2 \omega^2}}$, $a = \frac{r_p}{Q}$

$$\frac{\partial |H(j\omega)|}{\partial \omega} = |G| \cdot \frac{-4\omega(r_p^2 - \omega^2) + 2a^2\omega}{[(r_p^2 - \omega^2)^2 + a^2\omega^2]^{3/2}} = 0 \Rightarrow$$

$$2(r_p^2 - \omega^2) = a^2 \Leftrightarrow \omega^2 = r_p^2 - \frac{a^2}{2} = r_p^2 - \frac{r_p^2}{2Q^2} = r_p^2 \left(1 - \frac{1}{2Q^2}\right)$$

$$\Leftrightarrow \omega = \omega_{\text{peak}} = \begin{matrix} + \\ - \end{matrix} r_p \sqrt{1 - \frac{1}{2Q^2}} \quad \left(\text{and } \omega = 0, \text{ corresp. to minimum when } 0 < \omega_{\text{peak}} < \infty \right)$$

d) $1 - \frac{1}{2Q^2} \geq 0 \Leftrightarrow Q \geq \frac{1}{\sqrt{2}}$

6a) $I_{op} = 0 \Rightarrow V_+ = 0$ and $V_{out} = A(V_+ - V_-) = -AV_-$

and $V_{in}(s) - I(s)(Z_1(s) + Z_2(s)) - V_{out}(s) = 0$ (1)

$I(s) = \frac{V_{in}(s) - V_-(s)}{Z_1(s)} = \frac{V_{in}(s)}{Z_1(s)} + \frac{V_{out}(s)}{Z_1(s)A(s)}$ (2) (from (1))

(1) & (2) $\Rightarrow V_{in}(s) - \left(\frac{V_{in}(s)}{Z_1(s)} + \frac{V_{out}(s)}{Z_1(s)A(s)} \right) (Z_1(s) + Z_2(s)) - V_{out}(s) = 0$

$\Leftrightarrow V_{in}(s) \left(1 - \frac{Z_1(s) + Z_2(s)}{Z_1(s)} \right) = V_{out}(s) \left(1 + \frac{Z_1(s) + Z_2(s)}{Z_1(s)A(s)} \right)$

$= -\frac{Z_2(s)}{Z_1(s)} \quad \left(\rightarrow 1 \text{ when } A \rightarrow \infty \right)$

$\Leftrightarrow H(s) = \frac{V_2(s)}{V_1(s)} = -\frac{Z_2(s)}{Z_1(s)} \cdot \frac{1}{1 + \frac{Z_1(s) + Z_2(s)}{Z_1(s)A(s)}}$

b) $\zeta = \frac{Z_2}{Z_1} \Rightarrow H(j\omega) = -\zeta \cdot \frac{1}{1 + \frac{1 + \zeta}{A(j\omega)}}$

$= -\zeta \cdot \frac{1}{1 + \frac{1 + \zeta}{A_0} \cdot \left(1 + \frac{j\omega}{\omega_0} \right)}$

$A_0 \gg \zeta \Rightarrow H(j\omega) \approx \frac{-\zeta}{1 + j \cdot \frac{(1 + \zeta)\omega}{A_0 \omega_0}}$

$|H(j\omega)| = |\zeta|, \quad |H(j\omega)| = \frac{|\zeta|}{\sqrt{2}} \text{ when } \frac{1 + \zeta}{A_0 \omega_0} \omega = 1$

$\Leftrightarrow \omega = \frac{A_0 \omega_0}{1 + \zeta} = \omega_{3dB}$

7) BP: $s + \frac{\omega_I^2}{s} - p = 0 \Leftrightarrow s^2 - p \cdot s + \omega_I^2 = 0$

poles at $\frac{p}{2} \pm \sqrt{\frac{p^2}{4} - \omega_I^2} = \left(p = -10, \omega_I^2 = 9 \right) = -5 \pm 4 = -9, -1$

zeros at $s = 0$ & $s = \infty$ ($s^2 + \frac{\omega_I^2}{s} - \infty = 0$)

BS: $\frac{\omega_I^2}{s + \frac{\omega_I^2}{s}} - p = 0 \Leftrightarrow \frac{\omega_I^2 s}{s^2 + \omega_I^2} - p = 0 \Leftrightarrow$

$\Leftrightarrow p s^2 - \omega_I^2 s + \omega_I^2 p = 0 \Leftrightarrow s^2 - \frac{\omega_I^2}{p} s + \omega_I^2 = 0$

\Rightarrow Poles at $\frac{\omega_I^2}{2p} \pm \sqrt{\left(\frac{\omega_I^2}{2p}\right)^2 - \omega_I^2}$

zeros at $s = \pm j \omega_I$

b) BP: $\frac{1}{sC} \rightarrow \frac{1}{\left(s + \frac{\omega_I^2}{s}\right)C} = \frac{1}{sC + \frac{\omega_I^2 C}{s}} \Leftrightarrow \frac{\omega_I^2 s}{s^2 + \omega_I^2} = \infty$
 $\Leftrightarrow s^2 + \omega_I^2 = 0$

$= \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$

with $\frac{1}{Z_1} = sC \Leftrightarrow Z_1 = \frac{1}{sC}$

$\frac{1}{Z_2} = \frac{\omega_I^2 C}{s} \Leftrightarrow Z_2 = \frac{s}{\omega_I^2 C} = sL$

with $L = \frac{1}{\omega_I^2 C}$

Impedance of parallel connection of Z_1 & Z_2