

Exam in TSTE14 Analog Filters

Exam code:	TEN1	
Date:	2016-06-09	Time: 14–18
Place:	TER4	
Examiner:	Håkan Johansson	
Department:	ISY	
Allowed aids:	Pocket calculator Wanhammar: Tables and formulas for analog and digital filters Söderkvist: Formler och Tabeller Ingelstam, Rönngren, Sjöberg: Tefyma Ekbohm: Tabeller och Formler NT Nordling: Physics Handbook for Science and Engineering Strid: Formler och Lexikon Mathematical tables	
Number of tasks:	7	
Grading:	Maximum 70 points, 30 points required to pass the exam. Note that a motivation/solution is required to get the maximal number of points for a problem. Note that 10, 8, 6, 4, or 2 points obtained at the seminars means that you do not have to solve Problem 1, 1(a)-(d), 1(a)-(c), 1(a)-(b), or 1(a), respectively.	
Solutions:	Will be published no later than three working days after the exam at http://www.commsys.isy.liu.se/en/student/kurser/TSTE14/	
Result:	Available by 2016-06-23	

- 1
- a. What is a main difference between passive and active components? (2 p)
 - b. What is a Richards structure? (2 p)
 - c. What are the potential drawbacks of using frequency transformations when designing bandpass and bandstop filters? (2 p)
 - d. Which of the following two filters requires most components (capacitors and inductors) in a ladder realization: an 11th-order Butterworth or a 7th-order Cauer? (2 p)
 - e. How are the poles and zeros related in an allpass filter? (2 p)
- 2 Synthesize a Cauer filter that meets the following specification: $\omega_c = 2\pi \times 2$ Mrad/s, $\omega_s = 2\pi \times 9.4$ Mrad/s, $A_{\max} = 0.01$ dB ($\rho = 5\%$), and $A_{\min} = 40$ dB. Determine the poles and zeros, and indicate their locations in the s -plane. The filter order should not be higher than necessary. (10 p)
- 3 Realize a Butterworth filter that meets the following specification: $\omega_c = 2\pi \times 10$ Mrad/s, $\omega_s = 2\pi$ Mrad/s, $A_{\max} = 0.2$ dB, and $A_{\min} = 40$ dB. Use a T -type ladder structure. Determine the capacitor and inductor values assuming source and load resistors with the same value according to $R_S = R_L = 10$ k Ω . (10 p)
- 4 Two transfer functions are given as

$$H_1(s) = \frac{p_1}{s + p_1}, \quad H_2(s) = \frac{s}{s + p_2}$$

- a. Determine the poles and zeros (expressed in terms of p_1 and p_2) of $H_3(s)$, as given below. (4 p)

$$H_3(s) = H_1(s) + H_2(s)$$

- b. Determine the poles and zeros (expressed in terms of p_1 and p_2) of $H_4(s)$, as given below. (4 p)

$$H_4(s) = H_1(s)H_2(s)$$

- c. Compute the magnitude responses of $H_3(s)$ and $H_4(s)$ for the angular frequencies $\omega = 0$ and $\omega = \infty$. (2 p)

- 5 a. Derive the transfer function $H(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$ for the active filter below, and show that it can be written as $H(s) = H_1(s)H_2(s)$ where


$$H_1(s) = \frac{sRC}{1 + sRC}, \quad H_2(s) = \frac{A(s)}{1 + A(s)}$$

with $A(s)$ being the transfer characteristics of the OP amplifier (that is, a non-ideal OP amplifier is assumed). (5 p)

- b. Sketch the magnitude responses of $H_1(s)$, $H_2(s)$, and $H(s)$, and indicate their 3dB angular frequencies. Use reasonable approximations if necessary. (For a filter $H(s)$, the 3dB angular frequency, say ω_{3dB} , is defined by $|H(j\omega_{3dB})| = G/\sqrt{2}$ where G represents the maximum value of $|H(j\omega)|$). Assume that $R = 1 \text{ k}\Omega$, $C = 100 \text{ nF}$, and

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

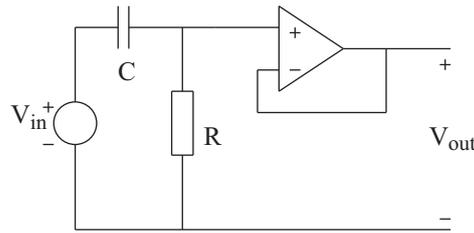with $A_0 = 10^5$ and $\omega_0 = 2\pi \times 10 \text{ rad/s}$. (5 p)



- 6 For a lowpass-to-bandpass frequency transformation

$$S = s + \frac{\omega_I^2}{s}$$

where $\omega_I^2 = \omega_{c1}\omega_{c2} = \omega_{s1}\omega_{s2}$, show that:

- a. The frequency responses are related as $H_{BP}(j\omega) = H_{LP}(j\Omega)$, where $\Omega = \omega - \omega_I^2/\omega$. (2 p)
- b. The passband region of the lowpass filter, $\Omega \in [-\Omega_c, \Omega_c]$ is mapped to the two passband regions of the bandpass filter, $\omega \in [\omega_{c1}, \omega_{c2}]$ and $\omega \in [-\omega_{c2}, -\omega_{c1}]$ where $\Omega_c = \omega_{c2} - \omega_{c1}$. Note that the passband regions given above include the negative frequencies. (8 p)

- 7 For a doubly resistively terminated LC -filter, seen in the figure below, derive the transfer function, defined by $H(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$, expressed in terms of R_S , R_L , $A(s)$, $B(s)$, $C(s)$, and $D(s)$, where $A(s)$, $B(s)$, $C(s)$, and $D(s)$ are the entries in the chain matrix of the two-port between R_S and R_L . (10 p)

