


# Solutions to ~~75TE14~~ <sup>75TE14</sup> Analog Filters 160321

a) Linear  $a_1 x_1(t) + a_2 x_2(t) \rightarrow a_1 y_1(t) + a_2 y_2(t)$  if  $x(t) \rightarrow y(t)$   
 Time-invariant  $x(t-t_0) \rightarrow y(t-t_0)$

b) LP: 2 zeros at  $s = \infty$ , BP: one zero at  $s = 0$   
 HP: 2 zeros at  $s = 0$ , one zero at  $s = \infty$

c) Overdesigned (higher filter order) due to band edge symmetries and the same attenuation in both passbands/stopbands  
 BP

d) Low sensitivity  $\Rightarrow$  small variations in  $H(j\omega)$  when component values deviates from nominal values

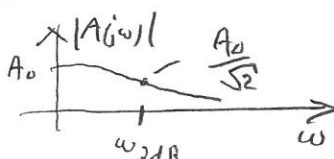e)  $\omega_z = A_0 \cdot \omega_{3dB}$    $A(j\omega) = \frac{A_0}{1 + j\frac{\omega}{\omega_{3dB}}}$

Approx. the max bandwidth of the filter in which the opamp is used

2) Filter order (nomogram  $\frac{\omega_s}{\omega_z} = 2$ )  $N = 5$

Table C05150,  $30 \leq \theta \leq 36$  Select  $\theta = 33$  (for ex)

Normalized poles:  
 $-0,6046827$   
 $-0,1335634 \pm j1,0725098$   
 $-0,4279530 \pm j0,7336827$

Normalized zeros  
 $\pm j1,9153952$   
 $\pm j2,9552877$   
 one at  $\infty$


Denormalize, mult by  $\omega_c \Rightarrow$

poles:  $-3,7993334 \times 10^6$   
 $(-0,8392036 \pm j6,7387778) \times 10^6$   
 $(-2,6889080 \pm j4,6098644) \times 10^6$

zeros  $\pm j1,2034783 \times 10^7$   
 $\pm j1,8568620 \times 10^7$   
 one at  $\infty$

3)  $\frac{LP \text{ prototype}}{\Omega_c} = \frac{\omega_I^2}{\omega_c} \left\{ \text{use } \omega_I^2 = \omega_c \right\} = 1, \quad \Omega_s = \frac{\omega_I^2}{\omega_s} = \frac{\omega_c}{\omega_s} = 5$


$\Rightarrow$  Filter order  $N=3$

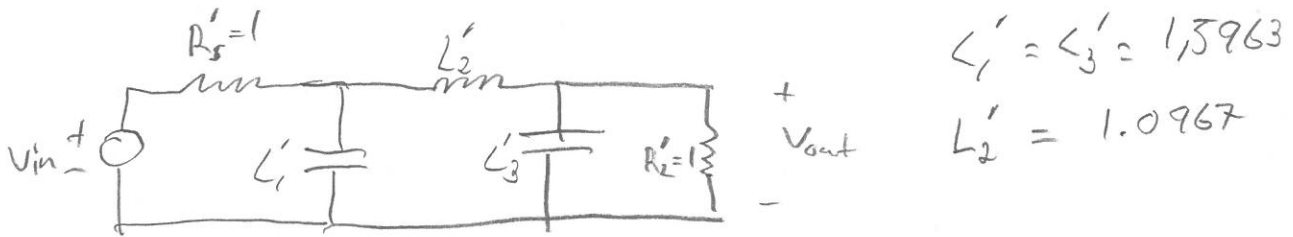

Denormalize with  $\Omega_c = 1, R = R_s = R_L = 2k\Omega \Rightarrow$

$L_1 = L_3 = \frac{C'_1}{\Omega_c \cdot R} = 0.79815 \text{ mF}, \quad L_2 = L'_2 \cdot \frac{R}{\Omega_c} = 2.1934 \text{ kH}$

LP  $\rightarrow$  HP

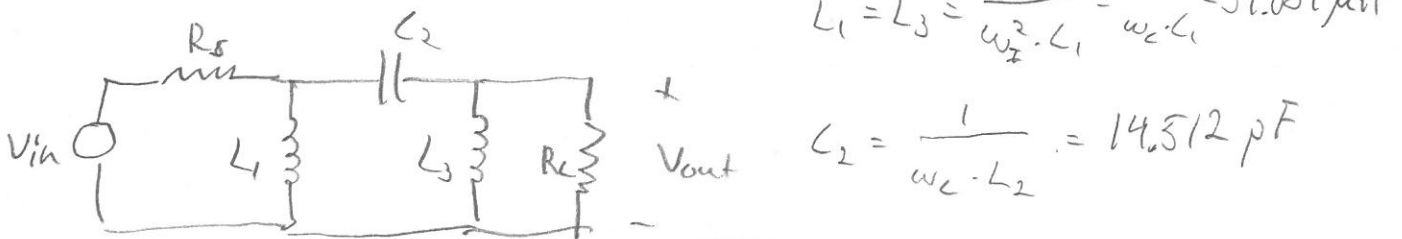

4) a) BP:  $a=c=0, b \neq 0, BS: a \neq 0, c \neq 0, b=0$

b)  $H(j\omega) = \frac{e}{(j\omega)^2 + d \cdot j\omega + e}, \quad |H(j\omega)| = \frac{|e|}{\sqrt{(e-\omega^2)^2 + d^2\omega^2}}$

$\frac{\partial |H(j\omega)|}{\partial \omega} = |e| \cdot \frac{2(e-\omega^2) \cdot -2\omega + 2d^2\omega}{((e-\omega^2)^2 + d^2\omega^2)^{1.5}} = 0$  when  $\omega=0$  here not the sol. / we want


and when  $-4(e-\omega^2) + 2d^2 = 0 \Leftrightarrow \omega^2 = e - \frac{d^2}{2} \Leftrightarrow \omega = \sqrt{e - \frac{d^2}{2}}$   
 $(\omega = -\sqrt{e - \frac{d^2}{2}}, |H(j\omega)| = |H(-j\omega)|)$

$\therefore \omega_{\text{peak}} = \sqrt{e - \frac{d^2}{2}}$

with  $e=10, d=1: \omega_{\text{peak}} = \sqrt{10 - \frac{1}{2}} \approx 3.082207$

$\Rightarrow |H(j\omega_{\text{peak}})| \approx 3.2025$

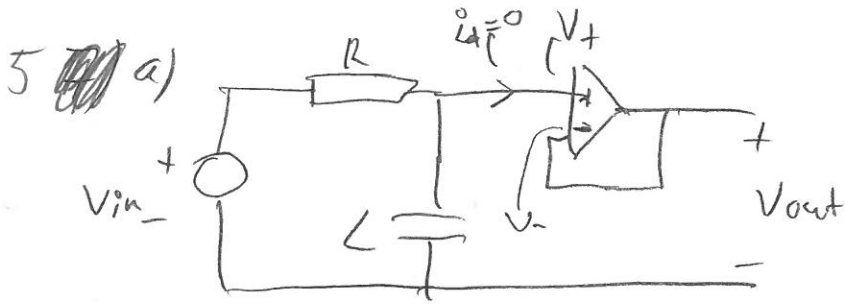(Note: with  $e=r_p^2, d=-2\sigma_p = \frac{r_p}{Q}: \omega_{\text{peak}} = r_p \sqrt{1 - \frac{1}{2Q^2}}$ )



$$V_{out}(s) = A(s) (V_+(s) - V_-(s)) \quad (1)$$

$$V_+(s) = V_{in}(s) - \frac{1/sC}{R + 1/sC} = V_{in}(s) \cdot \frac{1}{1 + sRC} \quad (2)$$

volt. div. since  $i_+ = 0$ , i.e.,  $i_R = i_C$

$$V_-(s) = V_{out}(s) \quad (3)$$

$$(1) - (3) \Rightarrow V_{out}(s) = A(s) (V_{in}(s) \cdot H_1(s) - V_{out}(s))$$


$$\Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{H_1(s) \cdot A(s)}{1 + A(s)} = H_1(s) H_2(s)$$

$$b) H_1(j\omega) = \frac{1}{1 + j\omega RC}, \quad \omega_{3dB}: \omega RC = 1 \Rightarrow \omega_{3dB} = \frac{1}{RC} = 1000 \text{ rad/s}$$

$$H_2(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)} = \frac{\frac{A_0}{1 + j\omega/\omega_0}}{1 + \frac{A_0}{1 + j\omega/\omega_0}} = \frac{A_0}{1 + A_0 + j\omega/\omega_0}$$

$$\omega_{3dB}: \frac{\omega}{\omega_0} = 1 + A_0 \approx \omega_{3dB} = \omega_0(1 + A_0) \approx \omega_0 A_0 = 2\pi \cdot 10^6 \text{ rad/s}$$

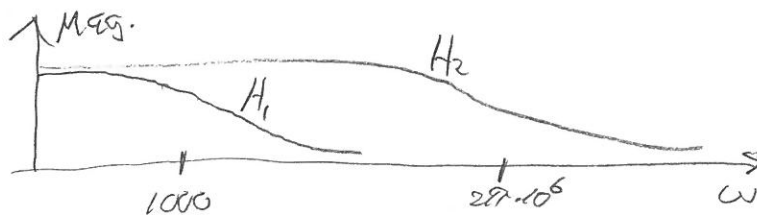$H(j\omega)$ :  $\omega_{3dB}$  approx the same as for  $H_1(j\omega)$  since the bandwidth of  $H_2(j\omega)$  much larger



$$6) a) H_{BP}(s) = H_{LP}(s') \text{ for } s' = s + \frac{\omega_I^2}{s}$$

$$s = j\omega \Rightarrow s' = j\omega + \frac{\omega_I^2}{j\omega} = j\left(\omega - \frac{\omega_I^2}{\omega}\right) = j\Omega \text{ for } \Omega = \omega - \frac{\omega_I^2}{\omega}$$

$$\therefore H_{BP}(j\omega) = H_{LP}(j\Omega) \text{ for } \Omega = \omega - \frac{\omega_I^2}{\omega}$$

$$b) \Omega = \omega - \frac{\omega_I^2}{\omega} \text{ and } \Omega_c = \omega_{c2} - \omega_{c1} \text{ and } \omega_I^2 = \omega_{c1}\omega_{c2}$$


$$\left. \begin{aligned} \omega = \omega_{c1}: \Omega &= \omega_{c1} - \frac{\omega_{c1}\omega_{c2}}{\omega_{c1}} = \omega_{c1} - \omega_{c2} = -\Omega_c \\ \omega = \omega_{c2}: \Omega &= \omega_{c2} - \frac{\omega_{c1}\omega_{c2}}{\omega_{c2}} = \omega_{c2} - \omega_{c1} = \Omega_c \\ \& \ \Omega = \omega - \frac{\omega_I^2}{\omega} \text{ increasing function on } [\omega_{c1}, \omega_{c2}] \end{aligned} \right\} (1)$$

$$\therefore \omega \in [\omega_{c1}, \omega_{c2}] \Leftrightarrow \Omega \in [-\Omega_c, \Omega_c]$$

$$\left. \begin{aligned} \omega = -\omega_{c1}: \Omega &= -\omega_{c1} + \frac{\omega_{c1}\omega_{c2}}{\omega_{c1}} = \omega_{c2} - \omega_{c1} = \Omega_c \\ \omega = -\omega_{c2}: \Omega &= -\omega_{c2} + \frac{\omega_{c1}\omega_{c2}}{\omega_{c2}} = \omega_{c1} - \omega_{c2} = -\Omega_c \\ \& \ \Omega = \omega - \frac{\omega_I^2}{\omega} \text{ increasing function on } [-\omega_{c2}, -\omega_{c1}] \end{aligned} \right\} (2)$$

Alt: (2) follows from (1) and the fact that
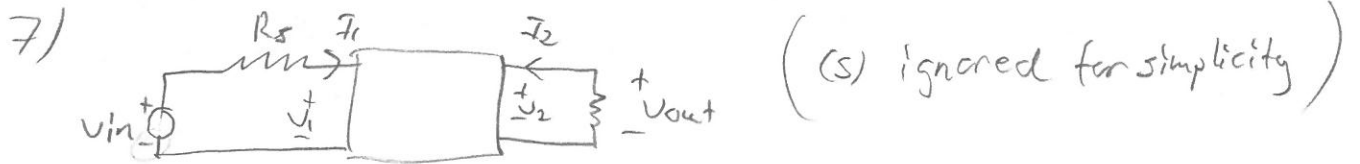
$$\omega \rightarrow -\omega \text{ corresponds to } \Omega \rightarrow -\Omega$$



$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} \quad (1)$$

$$V_2 = v_{out} = -R_L I_2 \quad (2)$$

$$v_{in} = V_1 + R_s I_1 \quad (3)$$

$$(1) \text{ and } (2) \Rightarrow \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} v_{out} \\ v_{out}/R_L \end{pmatrix} \quad (4)$$

$$(3) \text{ and } (4) \Rightarrow v_{in} = \left( A + \frac{B}{R_L} + C R_s + D \cdot \frac{R_s}{R_L} \right) v_{out}$$

$$\Rightarrow H = \frac{v_{out}}{v_{in}} = \frac{1}{A + \frac{B}{R_L} + C R_s + D \frac{R_s}{R_L}} = \frac{R_L}{A R_L + B + C R_L R_s + D R_s}$$