

1a) Passive - can only dissipate power
 \Rightarrow Passive filters always stable


b) Cascaded two-ports

c) Overdesigned (higher filter order) due to band edge symmetries and the same attenuation in both passbands/stopbands.
BS BP

d) 11th-order Butterworth - 11 components
7th-order Chebyshev - 10 components

e) $z = p$ mirrored, $z = a + jb$, $p = -a + jb$

Ex second-order

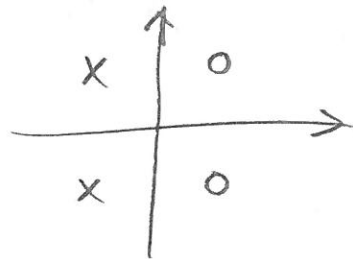

2) Filter order (Nomogram $\frac{\omega_s}{\omega_c} = 4,7$) $N = 4$
 Table C04050b) $14 \leq \Theta \leq 23$ Select $\Theta = 18$ (for ex.)

Normalized poles (rounded)
 $-0,3749 \pm j1,3374$
 $-0,9954 \pm j0,5928$

zeros $\pm j3,8206$
 2 at ∞

Denormalize, mult. by $\omega_c \Rightarrow$

poles $(-4,711 \pm j16,8062) \times 10^6$


$(-12,5086 \pm j7,4493) \times 10^6$

zeros $48,0111 \times 10^6$

2 at ∞

3) LP prototype $\Omega_c = \frac{\omega_F^2}{\omega_c} = 1$ (use $\omega_F^2 = \omega_c$), $\Omega_s = \frac{\omega_s^2}{\omega_c} = 10$

Filter order (Nomogram) $N = 3$

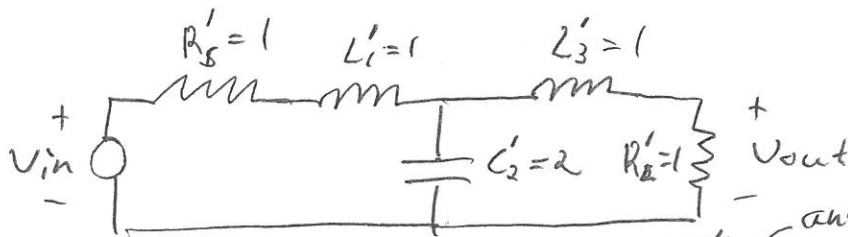


Denormalize with $\Omega_c \cdot \Sigma^{-1/3}$, $A_{max} = 10 \cdot \log_{10}(1 + \epsilon^2) = 0,2$
 $\epsilon = \sqrt{10^{0,1 A_{max}} - 1} = 0,2171 \Rightarrow \epsilon^{-1/3} = 1,664$

$\Rightarrow L_1 = L_3 = 6,040 \text{ kH}, C_2 = 0,1202 \text{ mF}$

LP \rightarrow HP

$$C_1 = C_3 = \frac{1}{\omega_F^2 L_1} = 2,648 \text{ pF}$$
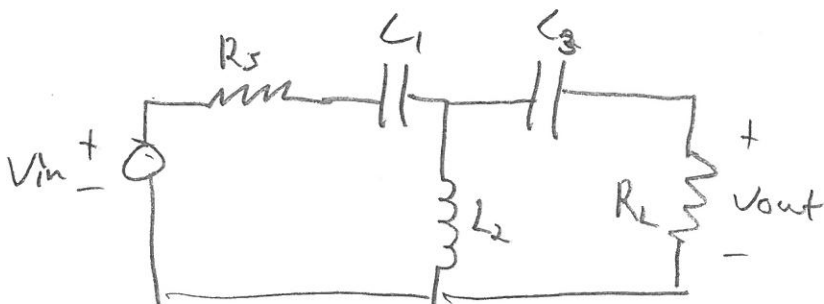
$$L_2 = \frac{1}{\omega_F^2 C_2} = 0,1324 \text{ mH}$$



$$4a) H_3(s) = \frac{P_1}{s+P_1} + \frac{s}{s+P_2} = \frac{P_1(s+P_2) + s(s+P_1)}{(s+P_1)(s+P_2)} = \frac{s^2 + 2P_1s + P_1P_2}{(s+P_1)(s+P_2)}$$

$$\text{poles: } -P_1 \text{ \& } -P_2$$

$$\text{zeros: } s = -\frac{P_1}{2} \pm \sqrt{\left(\frac{P_1}{2}\right)^2 - P_1P_2}$$


$$b) H_4(s) = \frac{P_1}{s+P_1} - \frac{s}{s+P_2} \quad \text{poles: } -P_1 \text{ \& } -P_2$$

$$\text{zero: } 0$$

$$c) |H_3(j0)| = |1+0| = 1, \quad |H_3(j\infty)| = |0+1| = 1$$

$$|H_4(j0)| = |1 \cdot 0| = 0, \quad |H_4(j\infty)| = |0 \cdot 1| = 0$$

5
a)

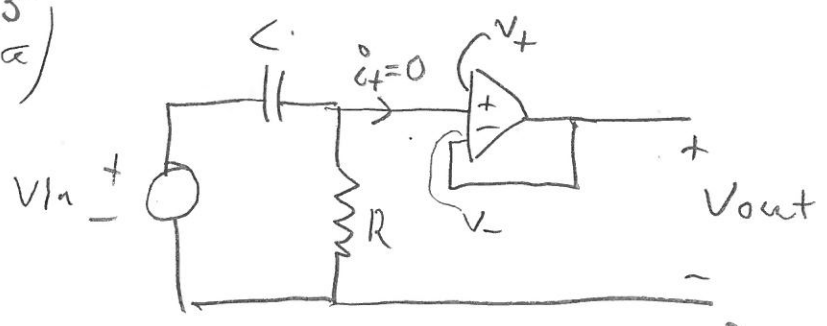

$$V_{out}(s) = A(s) (V_+(s) - V_-(s)) \quad (1)$$

$$V_+(s) = V_{in}(s) \cdot \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} \cdot V_{in}(s) \quad (2)$$

↑
voltage div. $H_1(s)$

$$V_-(s) = V_{out}(s) \quad (3)$$

$$(1) - (3) \Rightarrow V_{out}(s) = A(s) (H_1(s) V_{in}(s) - V_{out}(s))$$

$$\Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{H_1(s) A(s)}{1 + A(s)} = H_1(s) H_2(s)$$



b) $H_1(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$, $\omega_{3dB} = \omega RC = 1 \Rightarrow \omega_{3dB} = \frac{1}{RC} = 10 \text{krad/s}$

max: $|H(j\omega)| = 1$

$$H_2(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)} = \frac{A_0}{1 + \frac{j\omega}{\omega_0}} = \frac{A_0}{1 + \frac{j\omega/\omega_0}{1 + A_0}}$$

$A_0 \gg 1$
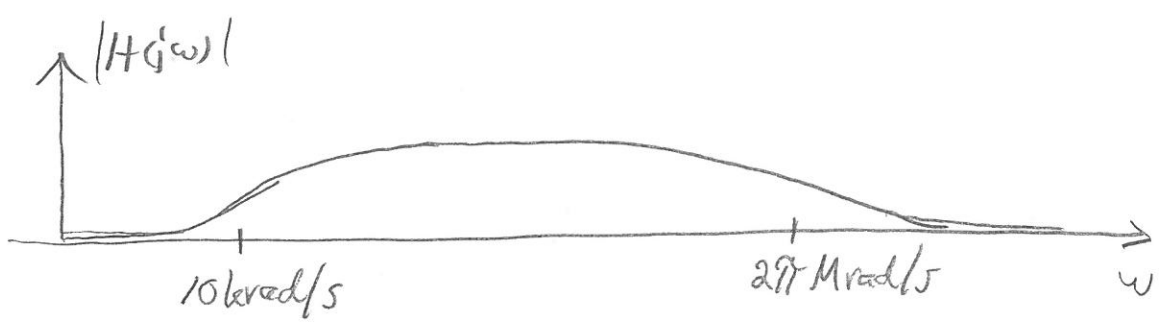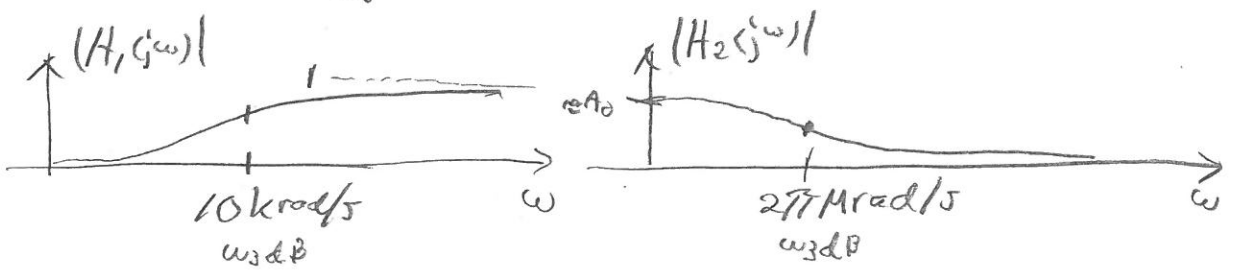
$$\omega_{3dB} : \frac{\omega}{\omega_0} = 1 + A_0 \Rightarrow \omega_{3dB} = \omega_0 (1 + A_0) \approx \omega_0 A_0 = 297 \text{Mrad/s}$$



$$b) a) H_{BP}(s) = H_{LP}(s') \text{ for } s' = s + \frac{\omega_I^2}{s}$$

$$s = j\omega \Rightarrow s' = j\omega + \frac{\omega_I^2}{j\omega} = j\left(\omega - \frac{\omega_I^2}{\omega}\right) = j\Omega \text{ for } \Omega = \omega - \frac{\omega_I^2}{\omega}$$

$$\therefore H_{BP}(j\omega) = H_{LP}(j\Omega) \text{ for } \Omega = \omega \pm \frac{\omega_I^2}{\omega}$$

$$b) \Omega = \omega - \frac{\omega_I^2}{\omega} \text{ and } \Omega_c = \omega_{c2} - \omega_{c1} \text{ and } \omega_I^2 = \omega_{c1}\omega_{c2}$$

$$\left. \begin{aligned} \omega = \omega_{c1}: \Omega &= \omega_{c1} - \frac{\omega_{c1}\omega_{c2}}{\omega_{c1}} = \omega_{c1} - \omega_{c2} = -\Omega_c \\ \omega = \omega_{c2}: \Omega &= \omega_{c2} - \frac{\omega_{c1}\omega_{c2}}{\omega_{c2}} = \omega_{c2} - \omega_{c1} = \Omega_c \\ \text{and } \Omega = \omega - \frac{\omega_I^2}{\omega} &\text{ increasing function on } [\omega_{c1}, \omega_{c2}] \end{aligned} \right\} (1)$$

$$\therefore \omega \in [\omega_{c1}, \omega_{c2}] \Leftrightarrow \Omega \in [-\Omega_c, \Omega_c]$$


$$\left. \begin{aligned} \omega = -\omega_{c1}: \Omega &= -\omega_{c1} + \frac{\omega_{c1}\omega_{c2}}{\omega_{c1}} = \omega_{c2} - \omega_{c1} = \Omega_c \\ \omega = -\omega_{c2}: \Omega &= -\omega_{c2} + \frac{\omega_{c1}\omega_{c2}}{\omega_{c2}} = \omega_{c1} - \omega_{c2} = -\Omega_c \\ \text{and } \Omega = \omega - \frac{\omega_I^2}{\omega} &\text{ increasing function on } [-\omega_{c2}, -\omega_{c1}] \end{aligned} \right\} (2)$$

$$\therefore \omega \in [-\omega_{c2}, -\omega_{c1}] \Leftrightarrow \Omega \in [-\Omega_c, \Omega_c]$$

Alt.: (2) follows from (1) and the fact that

$$\omega \rightarrow -\omega \text{ corresponds to } \Omega \rightarrow -\Omega$$

7)

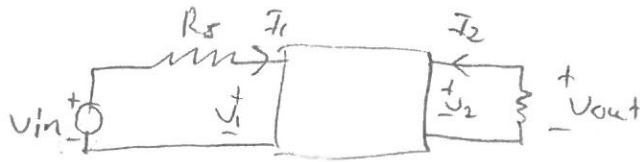

(s) ignored for simplicity

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} \quad (1)$$

$$V_2 = V_{out} = -R_L I_2 \quad (2)$$

$$V_{in} = V_1 + R_s I_1 \quad (3)$$

$$(1) \text{ and } (2) \Rightarrow \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{out} \\ V_{out}/R_L \end{pmatrix} \quad (4)$$

$$(3) \text{ and } (4) \Rightarrow V_{in} = \left(A + \frac{B}{R_L} + C R_s + D \cdot \frac{R_s}{R_L} \right) V_{out}$$

$$\Rightarrow H = \frac{V_{out}}{V_{in}} = \frac{1}{A + \frac{B}{R_L} + C R_s + D \frac{R_s}{R_L}} = \frac{R_L}{A R_L + B + C R_s R_L + D R_s}$$